

The Twelfth-Wave Matching Transformer

by

Darrel Emerson.


(This is a summary. Last modified May 25 1997)

The full article appeared in QST, Vol 81, No.6,
June 1997, pp.43-44, published by the ARRL.


The Twelfth-Wave Transformer is often a more convenient alternative to the more well-known quarter-wave transformer. It is not a new concept, being first published in 1961, but it is relatively unknown in amateur radio circles.

With the quarter-wave transformer, two impedances Z_1 and Z_2 are matched by using a quarter-wave of transmission line of characteristic impedance $\sqrt{Z_1 Z_2}$. This works well, but often requires a non-standard characteristic impedance. For example, to match a 50-ohm load to 75-ohm cable, a quarter-wave transformer needs a length of cable of characteristic impedance 61.2 ohms.

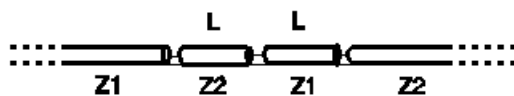With the twelfth-wave transformer, two lengths of cable are used in series, each electrically nearly one twelfth-wavelength, but of characteristic impedances equal to the two impedances Z_1 and Z_2 being matched. The figures below illustrate the difference between the twelfth-wave and a quarter-wave transformer.



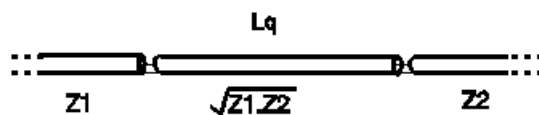The above figure illustrates the Twelfth-Wave transformer. To match impedances Z_1 and Z_2 , two lengths of cable are needed, each of length L close to one electrical twelfth-wavelength. The characteristic impedance of one length is Z_1 , of the other Z_2 .



As illustrated above, with the quarter-wave transformer, only one matching cable is required, of electrical length L_q =one quarter wavelength, but this is very often a non-standard characteristic impedance.

The precise length of a twelfth-wave section


The precise electrical lengths needed in the twelfth-wave transformer are just slightly less than an exact twelfth. When

matching impedances Z_1 and Z_2 , if $B=Z_1/Z_2$, then the precise electrical length of the "twelfth"-wave section is given by:

$$L = [\arctan(\sqrt{B/(B^2 + B + 1)})]/(2\pi)$$


where the arctan function is assumed to return an angle in radians. L is the electrical length of each section of matching cable, measured in wavelengths.

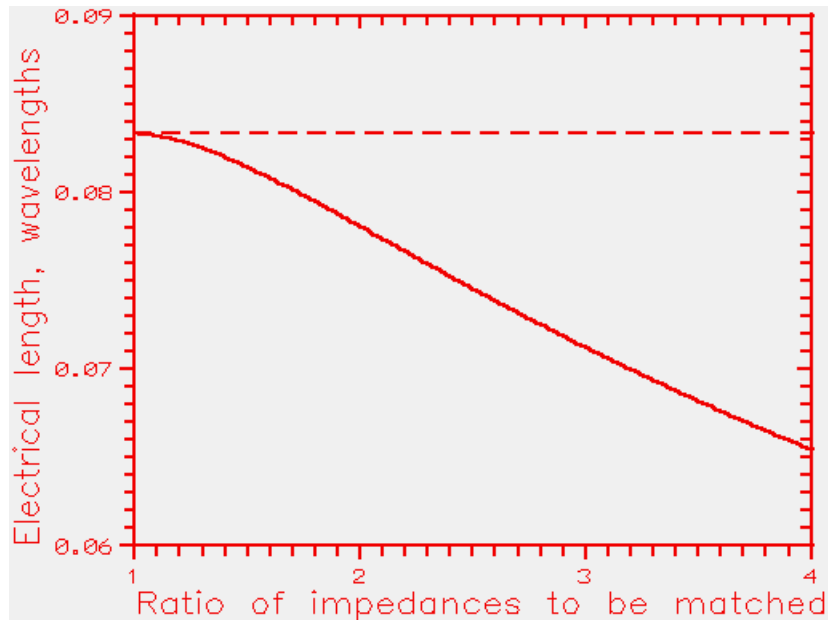The length L is plotted below as a function of the impedance matching ratio, Z_1/Z_2 . The horizontal dashed line corresponds to an exact twelfth length (0.0833333).



Bandwidth

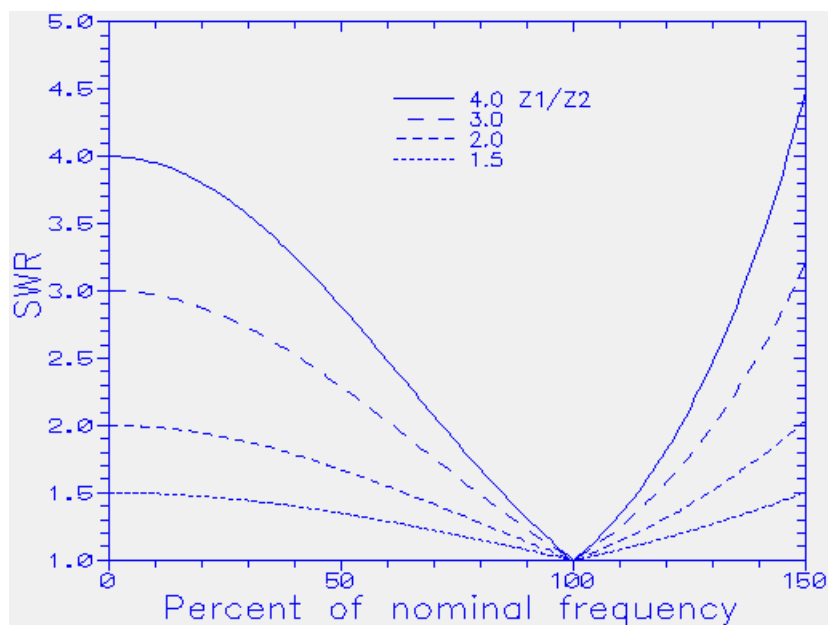
The SWR bandwidth of the twelfth-wave transformer is very broad, and is comparable to the quarter-wave transformer. The plot below shows the resulting SWR as a function of frequency, where a twelfth-wave transformer is used to match impedance ratios Z_1/Z_2 of 1.5, 2, 3 and 4. The frequency axis extends from D.C. to 50% higher than the nominal design frequency.



Examples

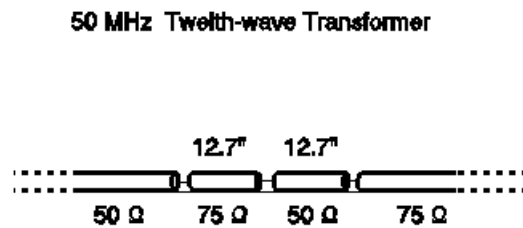(1) A twelfth-wave matching transformer for 50 MHz


A transformer for 50 MHz, matching 75 to 50 ohms: From the figure, or the equation, the required length of matching section is 0.0815 wavelengths. At 50 MHz (=6-meter wavelength) this becomes 0.489 meters. Allowing for a velocity factor of 0.66, the physical length becomes 0.323 meters, or 12.7 inches. The figure below illustrates the complete transformer.



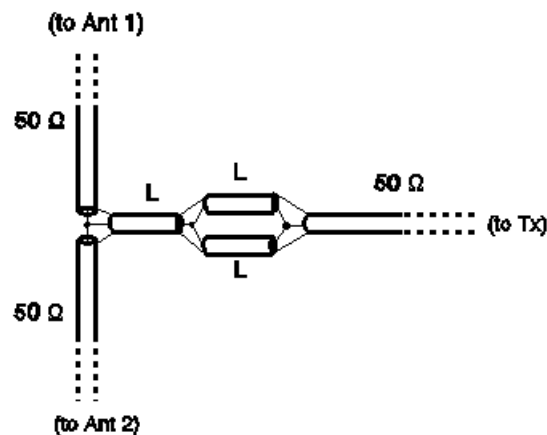(2) Matching several equal impedances Z_0 , in parallel, to Z_0 impedance cable

Suppose we wish to match two elements of a phased array, individually fed by a matched 50-ohm cable. Putting the two feeders to the individual elements in parallel gives a combined impedance of 25 ohms. To match this 25-ohm impedance to conventional 50-ohm cable, we need a length of 50-ohm, and a length of 25-ohm cable. The 25-ohm length can be constructed by putting two 50-ohm lengths in parallel. The figure below shows the general arrangement.

Matching two 50-ohm antennas to a single 50-ohm feeder



In the above figure, since we are matching an impedance ratio of 2:1, each length L is (from the above equation or the figure given the required length of matching section for a given transformation ratio) 0.0781 wavelengths. If this were to be used at 28 MHz (10.7 meters) the length becomes 0.836 meters. Allowing for a velocity factor of 0.66, this becomes a physical length of 0.552 meters or 21.7 inches. All lengths L would be 21.7 inches, and all cables are of the same (e.g. 50 ohm) characteristic impedance..

Note that this is a perfectly general way of solving the matching problem of putting N feeders, each of impedance Z_0 , in parallel. The required matching section impedances are Z_0 , and Z_0/N . It is always possible to make a feeder of characteristic impedance Z_0/N simply by putting N sections of impedance Z_0 in parallel.

Reference

Although relatively unknown in amateur radio circles, the twelfth-wave transformer was first described in 1961, when it was in use for matching 200 MHz components at the CERN accelerator. See:

"A Convenient Transformer for Matching Coaxial Lines"
by B. Bramham, in Electronic Engineering, Vol 33, pp.42-44,
January 1961.

[Feedback from readers on the "Twelfth-Wave Transformer"](#)

Since the appearance of the article in the June 1997 QST, I have received some correspondence from QST readers asking for further clarification on the use of the Twelfth-Wave Transformer. In the hope that it may help others, replies given to readers can be found on this link.

[Darrel Emerson top page](#)

